

**DEPARTEMEN PENDIDIKAN NASIONAL**  
**UNIVERSITAS PENDIDIKAN INDONESIA**  
**FAKULTAS PENDIDIKAN TEKNOLOGI DAN KEJURUAN**  
**JURUSAN PENDIDIKAN TEKNIK ELEKTRO**  
**(ELEKTRONIKA TELEKOMUNIKASI)**

---

**PRAKTIKUM TELEKOMUNIKASI II      FILTER:      JOBSHEET. 2**

---

**CHEBYCHEV dan BUTTERWORTH FILTER**


**TUJUAN:**

Dengan praktikum ini diharapkan mahasiswa dapat mengenal lebih jauh tentang filter jenis lain, antara lain di sini adalah Chebychev Filter. Mahasiswa juga mengenal dan dapat merancang serta mengaplikasikan filter ini pada aplikasi dilapangan.

**MATERI:**


The goal of this lab was to build a 600 KHz Chebyshev high pass RF filter of 7th order (3dB). Chebyshev filters feature superior attenuation in the stop band at the expense of ripple in the pass band. The Chebyshev response has the fastest rate of phase change compared to the Bessel and Butterworth filters. The trade off for this is that the Chebyshev filter has the longest group delay in the same comparison.

Gambaran:

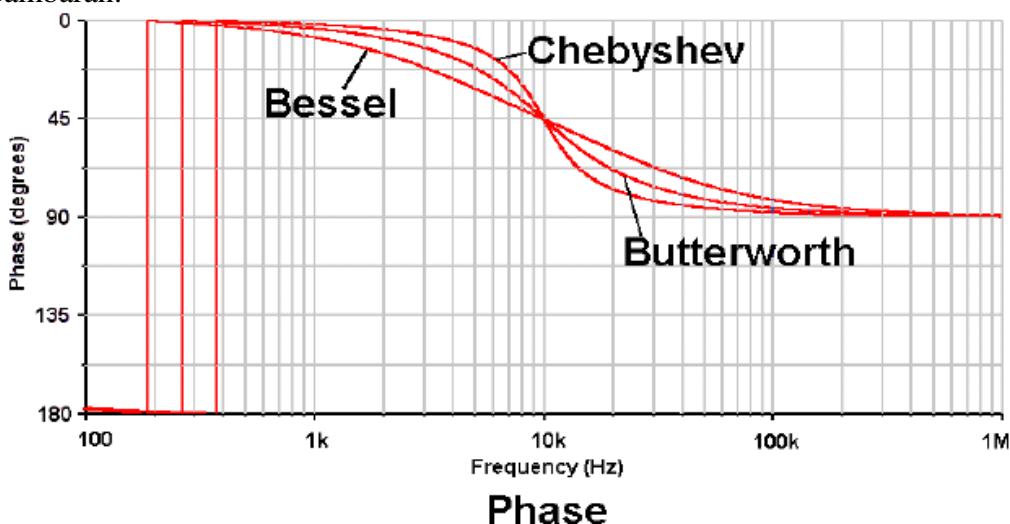

A graph of the phase change of a Chebyshev filter compared to the a Bessel and Butterworth Filters<sup>1</sup>

Gambaran lain adalah:

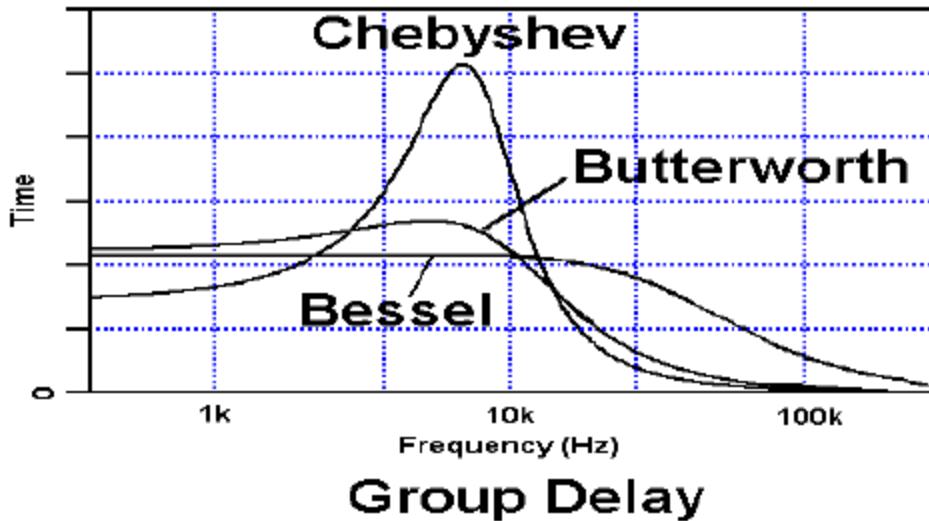

- This graph shows the group delay of the Chebyshev filter vs. the Butterworth and Bessel filters<sup>1</sup>

Implementasi sederhana bisa sbb:

## 7th Order High Pass Chebyshev I

Pass Band Frequency = 600.0 KHz  
 Pass Band Ripple = 3.000 dB

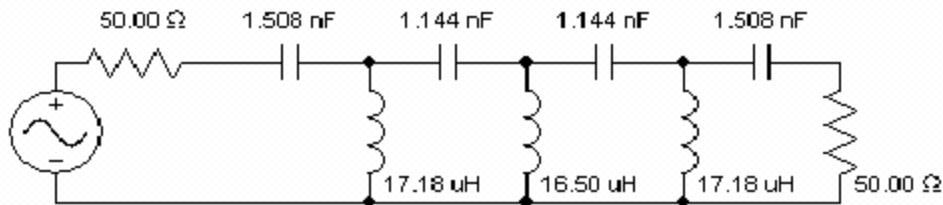


Figure 3 – Initial schematic

## 7th Order High Pass Chebyshev I

Pass Band Frequency = 600.0 KHz  
 Pass Band Ripple = 3.000 dB


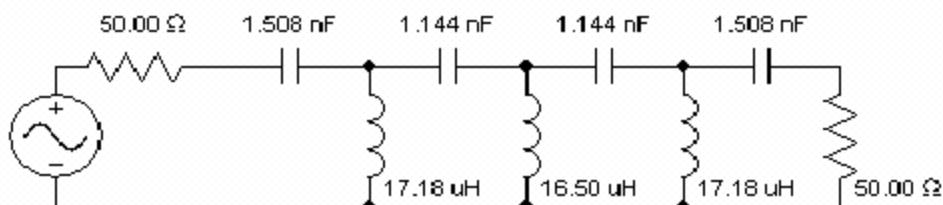


Figure 3 – Initial schematic

Atau dengan modifikasi:

## 7th Order High Pass Chebyshev I

Pass Band Frequency = 600.0 KHz  
Pass Band Ripple = 3.000 dB

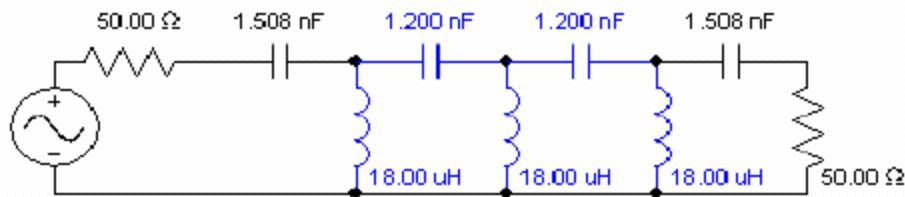


**Figure 4 – Modified schematic**

Spesifikasinya misanya sebagai berikut:

<b>Chebyshev I High Pass Filter</b>	
Pass band frequency	600 kHz
Pass band ripple	3.0 dB
Impedance	50Ω

**Table 1- Filter specifications**

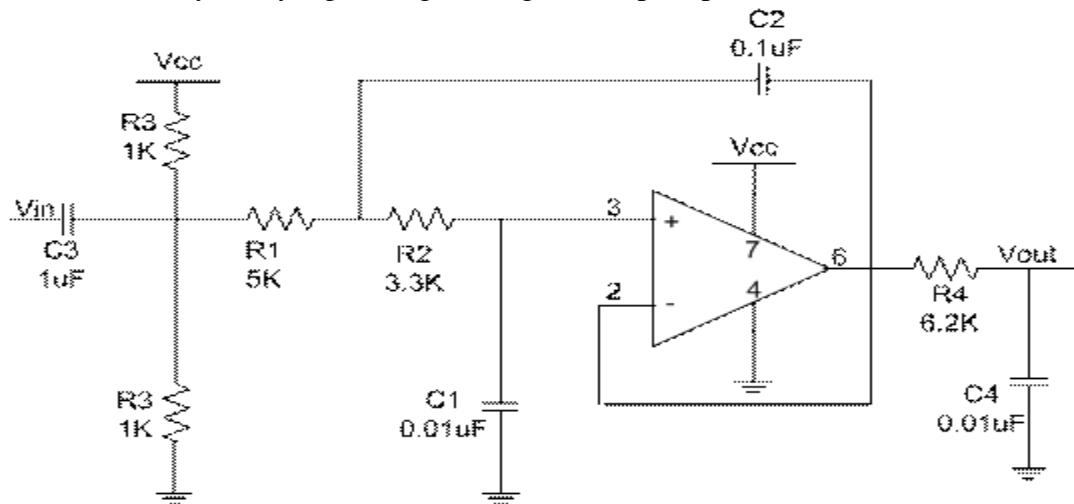Gambaran Chebyshev yang dibangun dengan IC OpAmp :



2 pole Chebyshev Filter followed by a single pole Butterworth Low pass filter

The filter consists of an Active Device (opamp) LMC7111 along with a combination of resistors and capacitors to provide the performance which is equivalent to LRC circuit at low frequency.

The transfer function of the low pass filter is equal to

$$A(s) = 1 / (1 + wc * C1 * (R1 + R2) * s + wc^2 * R1 * R2 * C1 * C2 * s^2)$$

Comparing this with standard transfer function we get  $A_0 = 1$ ,  $a_1 = wc * C1 * (R1 + R2) * s$ ,  $b_1 = wc^2 * R1 * R2 * C1 * C2$ .

So we pick the value of  $C1 = 0.01\mu F$ .  $C2 \geq C1 * 4 * b_1 / a_1^2$ . So we get  $C2 \geq .07\mu F$ . So we decided  $C2 = 0.1\mu F$ . Calculating  $R1$  and  $R2$  we get  $R1 = 620$  ohms and  $R2 = 3.3K$  ohms. But now  $R1$  in parallel with 2  $R3$ 's becomes very small. So a higher value than calculated was put for  $R1$  to get less ringing.

The component values of  $R4$  and  $C4$  were selected using the  $2 * \pi * f_c = 1 / (R4 * C4)$ . We picked an available value of  $C$  which was  $0.01\mu F$  and  $R4$  was found out to be  $6.2k$  for a cutoff frequency of  $2.6\text{ kHz}$ .

Untuk filter lolos rendah Butterworth dapat kita reviu dan buat sebagai berikut:  
Tentang IC pendukungnya (LMF 100):

### **General Description**


The LMF100 consists of two independent general purpose high performance switched capacitor filters. With an external clock and 2 to 4 resistors, various second-order and first-order filtering functions can be realized by each filter block. Each block has 3 outputs. One output can be configured to perform either an allpass, highpass, or notch function. The other two outputs perform bandpass and lowpass functions. The center frequency of each filter stage is tuned by using an external clock or a combination of a clock and resistor ratio. Up to a 4th-order biquadratic function can be realized with a single LMF100. Higher order filters are implemented by simply cascading additional packages, and all the classical filters (such as Butterworth, Bessel, Elliptic, and Chebyshev) can be realized. The LMF100 is fabricated on National Semiconductor's high performance analog silicon gate CMOS process, LMCMOST™. This allows for the production of a very low offset, high frequency filter building block. The LMF100 is pin-compatible with the industry standard MF10, but provides greatly improved performance.

### **Features**

- Wide 4V to 15V power supply range
- Operation up to 100 kHz
- Low offset voltage: typically (50:1 or 100:1 mode):  $V_{os1} = \pm 5\text{ mV}$ ,  $V_{os2} = \pm 15\text{ mV}$
- $V_{os3} = \pm 15\text{ mV}$
- Low crosstalk -60 dB


- Clock to center frequency ratio accuracy  $\pm 0.2\%$  typical
- $f_0 \times Q$  range up to 1.8 MHz
- Pin-compatible with MF10
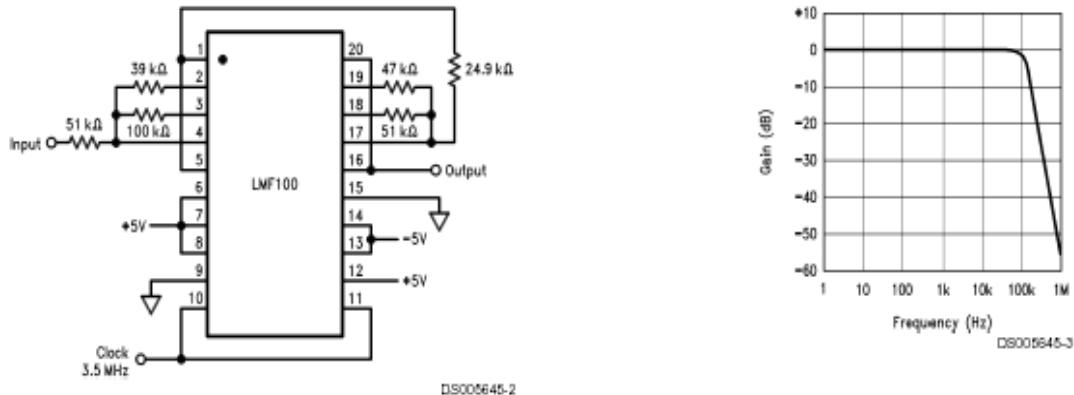
## 4th Order 100 kHz Butterworth Lowpass Filter



## Connection Diagram

Surface Mount and Dual-In-Line Package

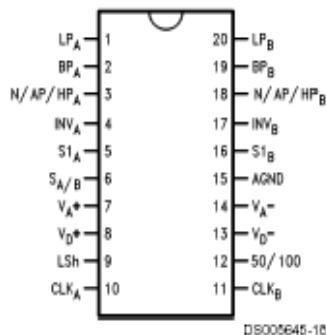

Top View  
Order Number  
LMF100CCN or LMF100CIWM  
See NS Package Number N20A or M20B

## PERALATAN DAN KOMPONEN YANG DIPERLUKAN

Siapkanlah peralatan :

1. Oscilloscope yang sesuai
  2. Signal Generator yang sesuai
  3. AVO/ Multimeter
  4. Breadboard 1 atau 2 buah
  5. Kabel-kabel/kawat-lawat seperlunya
  6. Solder dengan timah dan perlengkapannya
  7. Tang/ pinzet
- Komponen-komponen yang diperlukan:

Enjang A. Juanda  
Elektro FPTK- UPI -Bandung

1. IC Op Amp seperti dapat dibaca pada gambar-gambar dibawah ini.
2. Beberapa kapasitor (sda)
3. Beberapa resistor (sda)
4. Beberapa induktor(sda)
5. Lain-lain jika diperlukan atau menghendaki variasi.

**JALANNYA PERCOBAAN:**

Bangunlah rangkaian-rangkaian percobaan sebagai berikut:

1. Percobaan 1:

- a. Berilah pada Vin tegangan dibawah 5 Volt dengan frekuensi bervariasi, dari yang terendah hingga tertinggi yang dimungkinkan.
- b. Ukurlah diterminal Vout dengan Oscilloscope yang bersesuaian juga
- c. Amati dan catat hasil-hasil percobaannya dengan mengisi tabel berikut:

No	Input: Signal Generator		Output: Oscilloscope		Keterangan
	Tegangan	Frekuensi	Tegangan	Frekuensi	
1					
2					
3					
4					
5					
6					
7					
8					
9					
10					

d. Coba gambarkan hasil percobaan diatas. Jelaskan tafsiran anda.

2. Percobaan 2:

- a. Susunlah percobaan sesuai gambar percobaan berikut:
- b. Lengkapi percobaan seperti langkah-langkah a dan c diatas.
- c. Isilah tabel hasil percobaan seperti pada c di atas.
- d. Gambarkanlah hasil-hasil percobaan itu.

3. Percobaan 3

- a. Susunlah percobaan sesuai gambar percobaan berikut:
- b. Ikuti langkah-langkah seperti percobaan di atas.

**TUGAS**

1. Bereskan kembali dan kembalikan alat serta komponen yang anda gunakan pada percobaan ini kepada petugas.
2. Bersihkan bekas percobaan dengan baik

3. Buatlah Laporan Sementara untuk dikumulkan kepada Dosen ybs, dan segeralah buat Laporan Akhirnya di rumah paling lama 2 hari setelah percobaan ini.